

# HW Assignment #4

Orhan Ibrahim Kish  
22003656

1)

a)  $S_I = -10 \text{ dBm}$

$$SNR_{dB} = S_{I,dB} - N_{I,dB} \Rightarrow N_{I,dB} = S_{I,dB} - SNR_{I,dB} \Rightarrow N_{I,dB} = -10 \text{ dBm} - 25 \text{ dB}$$

$$\Rightarrow N_{I,dB} = -115 \text{ dBm}$$

$$\frac{SNR_I}{SNR_0} = 1 + \frac{kT_0B}{N_I} (f_m)$$

$$N_I = 10^{-11.5} \text{ W}$$

b)  $SNR_0 = \frac{SNR_I}{1 + \frac{kT_0B}{N_I} (f_m)} \Rightarrow f = 10^{0.5}$

$$\Rightarrow N_I = 3.16 \times 10^{-15} \text{ W}$$

$$SNR_0 = 111.4 = 20.46 \text{ dB}$$

b)  $S_I = -70 \text{ dBm} \Rightarrow N_{I,dB} = -105 \text{ dBm} \Rightarrow N_I = 3.16 \times 10^{-14} \text{ W}$

$$SNR_0 = 845.88 = 29.27 \text{ dB}$$

c)  $S_I = -60 \text{ dBm} \quad N_{I,dB} = -95 \text{ dBm} \Rightarrow N_I = 3.16 \times 10^{-13} \text{ W}$

$$SNR_0 = 2482.47 = 33.94 \text{ dB}$$

d)  $f = \frac{SNR_I}{SNR_0}$  if not only of  $N_I$  is at  $T = 290^\circ \text{K}$

$$f_{dB} = SNR_{I,dB} - SNR_{0,dB} \Rightarrow SNR_{I,dB} = 40 \text{ dB}$$

$$SNR_I = \frac{S_I}{N_I} = \frac{S_I}{kT_0B} = 10^4$$

$$\Rightarrow S_I = 4.002 \times 10^{-10} = -93.97 \text{ dBm}$$

$$2) F = F_{\max} + 4 \cdot r_n \frac{|P_s - P_{\text{opt}}|^2}{(1 - |P_s|^2)(1 + |P_{\text{opt}}|^2)}$$

Plug in the values.


$$F_{\max} = 10^{0.13} = 1.348$$

$$P_s = \frac{50 - 50}{50 + 50} = 0$$

$$F = 1.348 = 2.423 \text{ dB}$$

b) New source  $r_n = 20 + j10$

$$P_s = -0.4 + j0.2$$

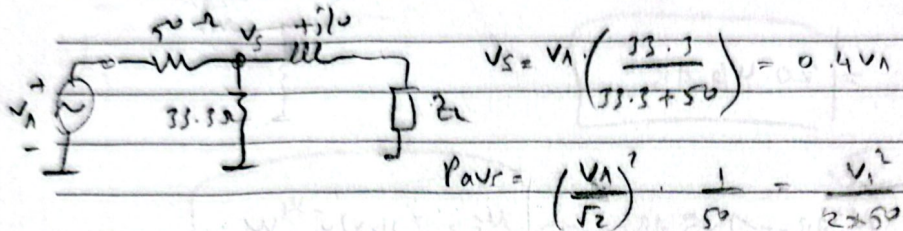

$$P_{\text{avr}} = \left( \frac{V_s}{\sqrt{2}} \right)^2 \cdot \frac{1}{20} = \frac{V_s^2}{2 \times 20}$$

$$G = \frac{P_{\text{avr}}}{P_{\text{avs}}} = \frac{(0.4 V_1)^2}{2 \times 20} \cdot \frac{2 \times 50}{V_1^2} = 0.4$$

$$\frac{T_{\text{eq}}}{R_{\text{eq}}} = \frac{T_{\text{so}}}{R_{\text{so}}} + \frac{T_{\text{added}}}{R_{\text{added}}} \Rightarrow \frac{290}{50} + \frac{300}{33.3} = \frac{T_{\text{eq}}}{20}$$

$$T_{\text{eq}} = 296.2 \text{ K}$$

$$F_1 = \frac{T_{\text{eq}}}{T_0 \cdot G} = \frac{296.2}{290 \cdot 0.4} = 2.55 = 4.07 \text{ dB}$$

Because we used perfect matching,  $F_2 = F_{\max} = 1.34 \text{ dB}$

$$F = F_1 + F_2 - 1 \Rightarrow F = 2.55 + \frac{10^{0.13} - 1}{0.4} = 3.42 = 5.34 \text{ dB}$$

$$c) P_{\text{sopt}} = -0.4 + j0.2 = \frac{Z_s - Z_0}{Z_s + Z_0} \Rightarrow Z_s = Z_0 \frac{1 + P_{\text{sopt}}}{1 - P_{\text{sopt}}} = 20 + j10$$

$$Y = G + jB \Rightarrow G = \frac{1}{20} = 0.02$$

Final value:  $\frac{1}{G + jB_c} + jX_L = 20 + j10$  (shunt capacitor + series inductor)

$$\Rightarrow \frac{1}{0.02 + jB_c} + jX_L = 20 + j10 \Rightarrow \frac{0.02 - jB_c}{(0.02)^2 + (B_c)^2} + jX_L = 20 + j10$$

$$\frac{50}{1.56 \text{ pF}} = 31.9 \text{ nH}$$

real part:  $\frac{0.02}{(0.02)^2 + (B_c)^2} = 20 \Rightarrow B_c = 0.02449$


$$jB_c = j\omega C \Rightarrow jC = \frac{B_c}{j\omega} = 1.56 \text{ pF}$$

$$X_L = \frac{B_c}{(0.02)^2 + (B_c)^2} = 10$$

$$X_L = 31.49 = \omega L \Rightarrow L = 2.19 \text{ nH}$$

3)

$$G_1 = 10 \text{ dB} \quad G_2 = 11 \text{ dB} \quad G_3 = 15 \text{ dB}$$

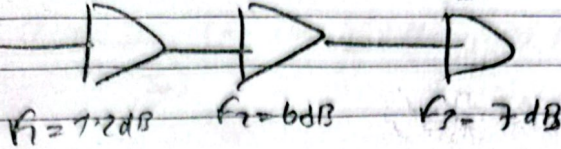Antenna  
 $B = 2 \text{ MHz}$ 

$$F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$

$$F = 10^{0.12} + \frac{10^{0.6} - 1}{10^1} + \frac{10^{0.7} - 1}{10^1 \cdot 10^{1.1}} = 1.648 \approx 2.17 \text{ dB}$$

$$N_0 = G_A k (T_{ant} + T_e) B$$

$$T_e = T_{e1} + \frac{T_{e2}}{G_1} + \frac{T_{e3}}{G_1 G_2} = (F - 1) T_0 = 187.9^\circ \text{K}$$

$$G_{A \text{ dB}} = G_1 + G_2 + G_3 \text{ dB} = 10 + 11 + 15 = 36 \text{ dB}$$

$$N_0 = -73 \text{ dBm} = 5.012 \times 10^{-15} \text{ W}$$


$$T_{ant} = \frac{N_0}{G_A k B} = 268.23^\circ \text{K}$$

4)

$$OZP3_1 = 25 \text{ dBm}$$

$$OZP3_2 = 32 \text{ dBm}$$

$$OZP3_3 = 40 \text{ dBm}$$

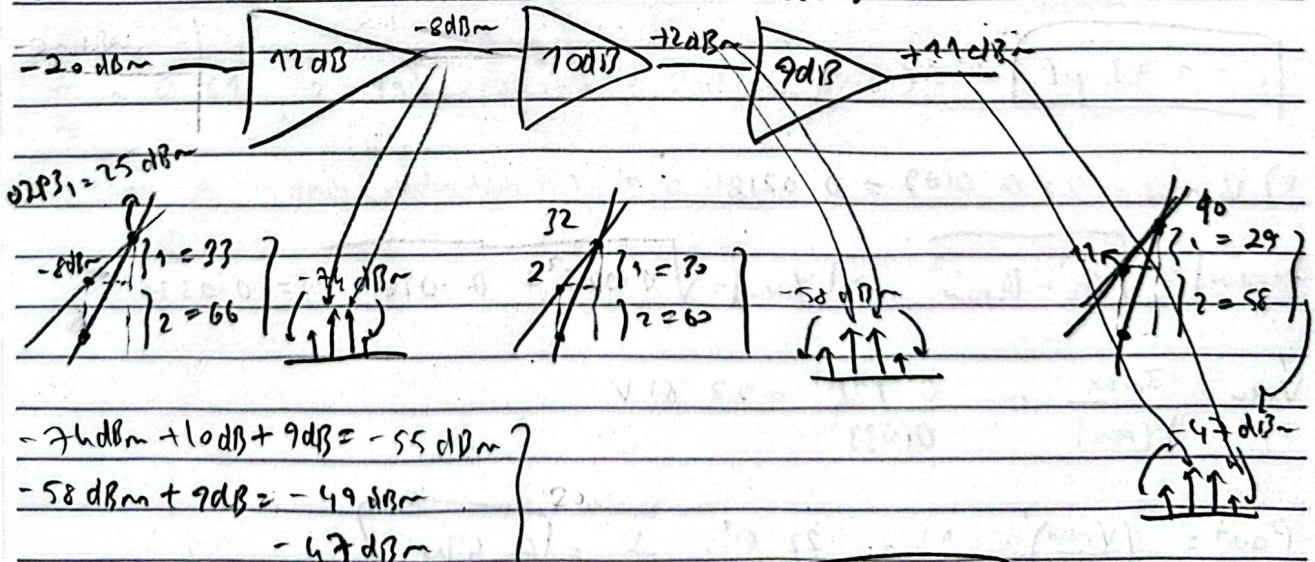

$$\begin{aligned} -7 \text{ dBm} + 10 \text{ dB} + 9 \text{ dB} &= -55 \text{ dBm} \\ -58 \text{ dBm} + 9 \text{ dB} &= -49 \text{ dBm} \\ &= -47 \text{ dBm} \end{aligned}$$

$$20 \log_{10} \left( 10^{-55/20} + 10^{-49/20} + 10^{-47/20} \right) = -40.18 \text{ dB}$$

$$5) V_{CC} - V_{SAT} = 28 - 0.5 = 27.5 \text{ V} = V_{peak}$$

$$a) I_Q = \frac{1.5 \text{ A}}{2} = 0.75 \text{ A} = I_{DC}$$

$$R_{opt} = \frac{V_{peak}}{I_{DC}} = \frac{27.5}{0.75} = 36.67 \Omega$$

$$b) P_{out} = \left[ \frac{1}{\sqrt{2}} \left( \frac{I_{max}}{2} \right) \right]^2 R_{opt} = \frac{1}{2} (0.75)^2 \cdot 36.67 = \boxed{10.31 \text{ W}}$$

$$c) R_{opt} = 36.67 \Omega \quad R_L = 40 \Omega$$

$R_L > R_{opt} \Rightarrow$  voltage is limited

$$\text{New current: } \frac{27.5}{40} = 0.6875 \text{ A}$$

$$P_{out} = \frac{V_{peak}^2}{2 R_L} = \left[ \frac{1}{\sqrt{2}} \left( \frac{I_{max}}{2} \right) \right]^2 \cdot R_L = \frac{1}{2} \cdot 0.6875^2 \cdot 40 = \boxed{9.45 \text{ W}}$$

$$d) G_{opt} = \frac{1}{R_{opt}} = \frac{1}{36.67} = 0.027$$

$$G_L = \frac{1}{R_L} = \frac{1}{40} = 0.025$$

$$Y_L = G_L + jB_L$$

$$B_L^2 = G_{opt}^2 - G_L^2$$

$$B_L \approx 0.0109$$

$$B_L = \frac{1}{X_C} \Rightarrow R_L = X_C \Rightarrow R_L = \omega C \Rightarrow C = \frac{B_L}{\omega} \Rightarrow C = \frac{0.0109}{2\pi \cdot 10^9}$$

$$\boxed{C = 1.73 \text{ pF}}$$

$$e) B_{new} = 2 \times 0.0109 = 0.0218$$

$$|Y_{new}| = \sqrt{G_L^2 + B_{new}^2} \Rightarrow |Y_{new}| = \sqrt{0.025^2 + 0.0218^2} = 0.033$$

$$V_{new} = \frac{I_{max}}{|Y_{new}|} = \frac{0.75 \text{ A}}{0.033} = 22.61 \text{ V}$$

$$P_{out} = \left( \frac{V_{new}}{\sqrt{2}} \right)^2 \cdot \frac{1}{R_L} = \frac{22.61^2}{2} \cdot \frac{1}{40} = \boxed{6.4 \text{ W}}$$

$$b) \alpha = 200^\circ \rightarrow \frac{\alpha}{2} = 100^\circ = 100 \times \frac{\pi}{180} = 1.745 \text{ radians}$$

$$I_1 = \frac{I_{max}}{2\pi(1 - \cos \frac{\alpha}{2})} (\alpha - \sin \alpha) \approx 0.52 \text{ A} \quad (I_{max} = 1 \text{ A})$$

↑  
fundamental component

$$V_{DD} = 28 - V_{SAT} = 28 - 0.5 = 27.5 \text{ V}$$

$$R_{opt} = \frac{V_{DD}}{I_1} = \frac{27.5}{0.52} = 52.9 \Omega$$

$$b) P_{out} = \left( \frac{V_{DD}}{\sqrt{2}} \right)^2 \cdot \frac{1}{R_{opt}} = 7.15 \text{ W}$$

$$P_{DC} = V_{DD} \cdot I_0 \Rightarrow I_0 = \frac{I_{max}}{2\pi} \frac{2 \sin \frac{\alpha}{2} - \alpha \cos \frac{\alpha}{2}}{1 - \cos \frac{\alpha}{2}} = 0.35 \text{ A}$$

$$P_{DC} = 27.5 \times 0.35 = 9.6 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{DC}} = 74.47\%$$

$$c) \text{ Normalized Gain} = \frac{I_1}{I_p} = \frac{\frac{I_{max}}{2\pi(1 - \cos \frac{\alpha}{2})} (\alpha - \sin \alpha)}{\frac{I_{max}}{(1 - \cos \frac{\alpha}{2})}} = \frac{\alpha - \sin \alpha}{2\pi}$$

$$\frac{I_1}{I_p} = 0.61 \rightarrow \text{gain reduction} = 20 \log_{10} (0.61) = \underline{\underline{-4.29 \text{ dB}}}$$

reduction

$$\text{In Class A, gain reduction} = 1 = \underline{\underline{0 \text{ dB}}}$$